

EE 371 Autumn 2016 - Lab 2

William Li, Dawn Liang, Jun Park

November 12, 2016

We certify that the work in this report is our own, and that any work that is not ours is cited.

William Li

Dawn Liang

Jun Park

Signature

Signature

Signature

Date

Date

Date

Contributions

Contents

1	Abstract	1
2	Introduction	1
3	Discussion	1
3.1	Design	1
3.1.1	Design Specification	1
3.1.2	Design Procedure	1
3.1.3	System Description	1
3.1.4	Software Implementation	1
3.1.5	Hardware Implementation	1
3.2	Test	1
3.2.1	Test Plan	1
3.2.2	Test Specification	1
3.2.3	Test Cases	1
4	Results	1
4.1	Analysis of Errors	1
5	Summary & Conclusion	1
6	Appendix	1
6.1	Two-scanner system	1
6.1.1	Verilog code	1
6.1.2	iverilog & gtkwave waveforms	29
6.1.3	Signal Tap II data	30
6.2	C Program	30

1 ABSTRACT

2 INTRODUCTION

3 DISCUSSION

3.1 Design

3.1.1 Design Specification

3.1.2 Design Procedure

3.1.3 System Description

3.1.4 Software Implementation

3.1.5 Hardware Implementation

3.2 Test

3.2.1 Test Plan

3.2.2 Test Specification

3.2.3 Test Cases

4 RESULTS

4.1 Analysis of Errors

5 SUMMARY & CONCLUSION

6 APPENDIX

6.1 Two-scanner system

6.1.1 Verilog code

```
// EE371 Lab3 Autumn 2016
// Authors: Dawn Liang, Jun Park, William Li
// Date:
//
// counter that counts every clock edge up/down to a min/max (0/10)
module counter(val, up, down, clk, reset);
    output [3:0] val;
    input up, down, clk, reset;

    // combinational logic: count every clock edge
    // min/max set at 0/10
    reg [3:0] ps, ns;
    always@(*) begin
        if (up && ~down && (ps < 4'b1010)) begin
            ns = ps + 1'b1;
        end else if (down && ~up && (ps > 4'b0)) begin
            ns = ps - 1'b1;
        end else begin
            ns = ps;
        end
    end
endmodule
```

```

        end
    end

    // output logic
    assign val = ps;

    // sequential logic; reset & next state
    always@(posedge clk) begin
        if (reset) begin
            ps <= 4'b0;
        end else begin
            ps <= ns;
        end
    end
endmodule

```

```

`include "counter.v"
module counter_testbench();
    reg up, down, clk, reset;
    wire [3:0] val;
    wire final_clock;

    counter dut (.val(val), .up(up), .down(down), .clk(clk), .reset(reset));

    // set up clock
    parameter CLOCK_PERIOD = 10;
    initial clk = 0;
    always begin
        #(CLOCK_PERIOD/2);
        clk = ~clk;
    end

    // begin simulation
    initial begin
        reset <= 1;          @(posedge clk);
                             @(posedge clk);
        reset <= 0; up <= 0; down <= 0;  @(posedge clk);
                                     @(posedge clk);
        up <= 1;              @(posedge clk); // 0
                                     @(posedge clk);
                                     @(posedge clk);
                                     @(posedge clk);
                                     @(posedge clk);
                                     @(posedge clk); // 5
                                     @(posedge clk);
                                     @(posedge clk);
                                     @(posedge clk);
                                     @(posedge clk); // 10
                                     @(posedge clk);
                                     @(posedge clk);
        down <= 1;          @(posedge clk);
        up <= 0;            @(posedge clk); // 10
                                     @(posedge clk);
                                     @(posedge clk);
                                     @(posedge clk);
                                     @(posedge clk);
    end

```

```

        @(posedge clk); // 5
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk); // 0
        @(posedge clk);
        down <= 0; @(posedge clk);
        @(posedge clk);

    $finish;
end

// gtkwave filedump
initial begin
    $dumpfile("counter.vcd");
    $dumpvars;
end
endmodule

```

```

// EE371 Lab 3 Autumn 2016
// Authors: Jun Park William Li Dawn Liang
// Date
//
// counter that counts up/down at different speeds depending on the state input

`include "clock_divider.v"
`include "counter.v"
module counterCtrl(val, state, clk, reset);
    input [2:0] state;
    input clk, reset;

    output [3:0] val;

    // state encodings
    parameter lowPower = 3'b000,
               standby = 3'b001,
               scanning = 3'b010,
               idle = 3'b011,
               xferring = 3'b100,
               flushing = 3'b101;

    // clock division
    wire [31:0] divided_clocks;
    clock_divider div (.divided_clocks(divided_clocks), .clk(clk));
    reg final_clock;

    // control signals
    reg up, down;
    always@(*) begin
        case (state)
            lowPower: begin
                final_clock = divided_clocks[0];
                up = 0; down = 0;
            end
            standby: begin
                final_clock = divided_clocks[0];
                up = 0; down = 0;
            end
        endcase
    end
endmodule

```

```

        scanning: begin                                // count up at 1x speed
            final_clock = divided_clocks[2];
            up = 1; down = 0;
        end
        idle: begin
            final_clock = divided_clocks[0];
            up = 0; down = 0;
        end
        xferring: begin                                // count down at 2x speed
            final_clock = divided_clocks[1];
            up = 0; down = 1;
        end
        flushing: begin                                // count down at 4x speed
            final_clock = divided_clocks[0];
            up = 0; down = 1;
        end
        default: begin
            final_clock = divided_clocks[0];
            up = 0; down = 0;
        end
    endcase
end

// counter
counter prog (.val(val), .up(up), .down(down), .clk(final_clock), .reset(reset));
endmodule

```

```

`include "counterCtrl.v"
module counterCtrl_testbench();
    reg [2:0] state;
    reg clk, reset;
    wire [3:0] val;

    counterCtrl dut (.val(val), .state(state), .clk(clk), .reset(reset));

    // set up clock
    parameter CLOCK_PERIOD = 10;
    initial clk = 0;
    always begin
        #(CLOCK_PERIOD/2);
        clk = ~clk;
    end

    initial begin
        reset <= 1;                                @(posedge clk);
                                                @(posedge clk);
        reset <= 0; state <= 3'b000; @(posedge clk); // lowPower
                                                @(posedge clk);
                                                @(posedge clk);
        state <= 3'b001; @(posedge clk); // standby
                                                @(posedge clk);
                                                @(posedge clk);
        state <= 3'b010; @(posedge clk); // scanning
                                                @(posedge clk);
                                                @(posedge clk);
                                                @(posedge clk);
                                                @(posedge clk);
                                                @(posedge clk);
    end
endmodule

```

```

        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        state <= 3'b011; @(posedge clk); // idle
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        state <= 3'b100; @(posedge clk); // xfer
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        state <= 3'b101; @(posedge clk); // flush
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
    $finish;
end

```



```

// gtkwave filedump
initial begin
    $dumpfile("counterCtrl.vcd");
    $dumpvars;
end
endmodule

```

```

// EE371 Lab3 Autumn 2016
// Authors: Dawn Liang, Jun Park, William Li
// Date:
//
// FSM controlling the state of the scanner
module scannerState(state, whichScanner, initialOn, goToStandby, startScan, prog,
    startTransfer, flush, clk, reset);
    output [2:0] state;
    input  whichScanner, initialOn, goToStandby, startScan, startTransfer, flush;
    input  [3:0] prog;
    input  clk, reset;

    // state encodings
    parameter lowPower = 3'b000,
        standby = 3'b001,
        scanning = 3'b010,
        idle = 3'b011,
        xferring = 3'b100,
        flushing = 3'b101;

    // combinational logic: next state
    reg [2:0] ps, ns;
    reg active = 0;
    always@(*) begin // cycling between scanners
        if (active) begin
            case (ps)
                lowPower: begin
                    if (goToStandby) ns = standby;
                    else ns = ps;
                end
                standby: begin
                    if (startScan) ns = scanning;
                    else ns = ps;
                end
                scanning: begin
                    if (prog == 4'b1010) ns = idle;
                    else ns = ps;
                end
                idle: begin
                    if (startTransfer) ns = xferring;
                    else if (flush) ns = flushing;
                    else ns = ps;
                end
                xferring: begin
                    if (prog == 4'b0) ns = lowPower;
                    else ns = ps;
                end
                flushing: begin
                    if (prog == 4'b0) ns = lowPower;
                    else ns = ps;
                end
            endcase
        end
    end
end

```

```

        default: ns = ps;
    endcase
end else begin // initialising: start the scanner cycles
    if (initialOn) begin
        active = 1;
        if (whichScanner) ns = scanning;
        else ns = lowPower;
    end else begin
        ns = lowPower;
    end
end
end

// output logic
assign state = ps;

// sequential logic: reset, next state
always@(posedge clk) begin
    if (reset) begin
        ps <= lowPower;
    end else begin
        ps <= ns;
    end
end
endmodule

```

```

`include "scannerState.v"
module scannerState_testbench();
    reg clk, reset;
    reg goToStandby, startScan, startTransfer, flush, initialOn;
    reg [3:0] prog;
    wire [2:0] state;

    // set up clock
    parameter CLOCK_PERIOD = 10;
    initial clk = 0;
    always begin
        #(CLOCK_PERIOD/2);
        clk = ~clk;
    end

    scannerState dut (.state(state), .initialOn(initialOn), .prog(prog),
        .goToStandby(goToStandby), .startScan(startScan),
        .startTransfer(startTransfer), .flush(flush), .clk(clk), .reset(reset));

    initial begin
        reset <= 1;
        reset <= 0; goToStandby <= 0; startScan <= 0; startTransfer <= 0; flush <= 0;
        initialOn <= 0; prog <= 4'b0;
        initialOn <= 1;
        goToStandby <= 1;
        goToStandby <= 0;
        startScan <= 1;
        startScan <= 0;

        @ (posedge clk);
        @ (posedge clk);
        @ (posedge clk);
        @ (posedge clk);
        @ (posedge clk);
        prog <=
    end

```

```

        4'b1010;@(posedge clk);
                                @(posedge clk);
                                @(posedge
                                clk);
        startTransfer <= 1;
        startTransfer <= 0;
                                prog <= 4'b0;
                                @(posedge clk);
                                @(posedge
                                clk);
        goToStandby <= 1;
        goToStandby <= 0; startScan <= 1;
                                prog <=
                                4'b1010;@(posedge clk);
                                flush <= 1;
                                flush <= 0;
                                clk);
                                prog <= 4'b0; @(posedge
                                clk);
                                @(posedge clk);

    $finish;
end

// gtkwave filedump
initial begin
    $dumpfile("scannerState.vcd");
    $dumpvars;
end
endmodule

```

```

`include "scannerState.v"
`include "counterCtrl.v"
module scanner(buffer_progress, state, readyToTransfer, otherGoToStandby,
    otherStartScan, otherFlush,
    whichScanner, initialOn, goToStandby, startScan, startTransfer, flush, clk,
    reset);
input clk, reset;
input initialOn, goToStandby, startScan, startTransfer, flush, whichScanner;

output readyToTransfer, otherGoToStandby, otherStartScan, otherFlush;
output [3:0] buffer_progress;
output [2:0] state;

    scannerState statedet (.state(state), .whichScanner(whichScanner),
        .initialOn(initialOn), .goToStandby(goToStandby), .startScan(startScan),
        .prog(buffer_progress), .startTransfer(startTransfer), .flush(flush), .clk(clk),
        .reset(reset));
    counterCtrl prog (.val(buffer_progress), .state(state), .clk(clk), .reset(reset));

    assign readyToTransfer = (buffer_progress == 5 && state == 3'b010);
    assign otherGoToStandby = (buffer_progress == 8 && state == 3'b010);
    assign otherStartScan = (buffer_progress == 9 && state == 3'b010);
    assign otherFlush = (buffer_progress == 5 && state == 3'b010);
endmodule

```

```

`include "scanner.v"
module scanner_testbench();
    reg clk, reset;
    reg initialOn, goToStandby, startScan, startTransfer, flush;
    wire readyToTransfer, otherGoToStandby, otherStartScan, otherFlush;
    wire [3:0] buffer_progress;
    wire [2:0] state;

```



```
@(posedge clk);
@ (posedge clk);
@ (posedge clk);
@ (posedge clk);
@ (posedge clk);
startTransfer <= 1;      @(posedge clk);
startTransfer <= 0;      @ (posedge clk);
                           @ (posedge clk);
                           @ (posedge clk);
                           @ (posedge clk);
                           @ (posedge clk);
                           @ (posedge clk);
```

[illegible]

```
@(posedge clk);
@(posedge clk);
```

```
startScan <= 0;
```

[illegible]


```

        $dumpfile("scanner.vcd");
        $dumpvars;
    end
endmodule

```

```

`include "scanner.v"
module overall(scan1_state, scan1_prog, scan2_state, scan2_prog,
    scan1_state_display, scan1_prog1_display, scan1_prog2_display,
    scan1_readyToTransfer,
    scan2_state_display, scan2_prog1_display, scan2_prog2_display,
    scan2_readyToTransfer,
    initialOn, startTransfer, clk, reset);
    input clk, reset;        // 50MHz clock, SW[0]
    input initialOn, startTransfer; // KEY[0], KEY[1]

    output reg [6:0] scan1_state_display, scan1_prog1_display, scan1_prog2_display, //
        HEX 2:0
        scan2_state_display, scan2_prog1_display, scan2_prog2_display; // HEX 5:3
    output scan1_readyToTransfer, scan2_readyToTransfer; // LED[0], LED[1]

    // HEX encodings 6543210
    parameter HEXS = 7'b0010010, // S s stands for Scanning state
        HEXt = 7'b0000111, // t t stands for transferring state
        HEXF = 7'b0001110, // F F stands for Flushing state
        HEXd = 7'b0100001, // d d stands for idle state
        HEXb = 7'b1111100; // b b stands for standby state

    parameter HEXOFF = 7'b1111111, // All segments are turned off
        HEXON = 7'b0000000; // All segments are turned on

    parameter HEX0 = 7'b1000000, // 0
        HEX1 = 7'b1111001, // 1
        HEX2 = 7'b0100100, // 2
        HEX3 = 7'b0110000, // 3
        HEX4 = 7'b0011001, // 4
        HEX5 = 7'b0010010, // 5
        HEX6 = 7'b0000010, // 6
        HEX7 = 7'b1111000, // 7
        HEX8 = 7'b0000000, // 8
        HEX9 = 7'b0010000; // 9

    // state encodings
    parameter lowPower = 3'b000,
        standby = 3'b001,
        scanning = 3'b010,
        idle = 3'b011,
        xferring = 3'b100,
        flushing = 3'b101;

    // 50 MHz clock division
    // wire [31:0] divided_clocks;
    // clock_divider cdiv (.divided_clocks(divided_clocks), .clk(clk));
    // reg final_clock = divided_clocks[22];

    // connecting wires
    output [3:0] scan1_prog, scan2_prog;
    output [2:0] scan1_state, scan2_state;
    wire scan1_otherGoToStandby, scan1_otherStartScan, scan1_otherFlush,

```

```

        scan2_otherGoToStandby, scan2_otherStartScan, scan2_otherFlush;

// 2 scanners
scanner scan1 (.buffer_progress(scan1_prog), .state(scan1_state),
    .readyToTransfer(scan1_readyToTransfer),
    .otherGoToStandby(scan1_otherGoToStandby), .otherStartScan(scan1_otherStartScan),
    .otherFlush(scan1_otherFlush),
    .whichScanner(1'b1), .initialOn(initialOn), .goToStandby(scan2_otherGoToStandby),
    .startScan(scan2_otherStartScan),
    .startTransfer(startTransfer), .flush(scan2_otherFlush), .clk(clk),
    .reset(reset));
scanner scan2 (.buffer_progress(scan2_prog), .state(scan2_state),
    .readyToTransfer(scan2_readyToTransfer),
    .otherGoToStandby(scan2_otherGoToStandby), .otherStartScan(scan2_otherStartScan),
    .otherFlush(scan2_otherFlush),
    .whichScanner(1'b0), .initialOn(initialOn), .goToStandby(scan1_otherGoToStandby),
    .startScan(scan1_otherStartScan),
    .startTransfer(startTransfer), .flush(scan1_otherFlush), .clk(clk),
    .reset(reset));

// output logic
always@(*) begin
    case (scan1_state)
        lowPower: begin
            scan1_state_display = HEXOFF;
            scan1_prog1_display = HEXOFF;
            scan1_prog2_display = HEXOFF;
        end
        standby: begin
            scan1_state_display = HEXb;
            scan1_prog1_display = HEX0;
            scan1_prog2_display = HEX0;
        end
        scanning: begin
            scan1_state_display = HEXS;
            case (scan1_prog)
                4'b0: begin // 0
                    scan1_prog1_display = HEX0;
                    scan1_prog2_display = HEX0;
                end
                4'b0001: begin // 1
                    scan1_prog1_display = HEX0;
                    scan1_prog2_display = HEX1;
                end
                4'b0010: begin // 2
                    scan1_prog1_display = HEX0;
                    scan1_prog2_display = HEX2;
                end
                4'b0011: begin // 3
                    scan1_prog1_display = HEX0;
                    scan1_prog2_display = HEX3;
                end
                4'b0100: begin // 4
                    scan1_prog1_display = HEX0;
                    scan1_prog2_display = HEX4;
                end
                4'b0101: begin // 5
                    scan1_prog1_display = HEX0;
                    scan1_prog2_display = HEX5;
                end
            end
        end
    endcase
end

```

```

        end
4'b0110: begin           // 6
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX6;
end
4'b0111: begin           // 7
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX7;
end
4'b1000: begin           // 8
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX8;
end
4'b1001: begin           // 9
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX9;
end
4'b1010: begin           // 10
    scan1_prog1_display = HEX1;
    scan1_prog2_display = HEX0;
end
default: begin
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX0;
end
endcase
end
idle: begin
    scan1_state_display = HEXd;
    scan1_prog1_display = HEX1;
    scan1_prog2_display = HEX0;
end
xferring: begin
    scan1_state_display = HEXt;
    case (scan1_prog)
4'b0: begin              // 0
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX0;
    end
4'b0001: begin           // 1
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX1;
    end
4'b0010: begin           // 2
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX2;
    end
4'b0011: begin           // 3
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX3;
    end
4'b0100: begin           // 4
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX4;
    end
4'b0101: begin           // 5
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX5;
    end
end

```

```

4'b0110: begin           // 6
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX6;
end
4'b0111: begin           // 7
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX7;
end
4'b1000: begin           // 8
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX8;
end
4'b1001: begin           // 9
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX9;
end
4'b1010: begin           // 10
    scan1_prog1_display = HEX1;
    scan1_prog2_display = HEX0;
end
default: begin
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX0;
end
endcase
end
flushing: begin
    scan1_state_display = HEXF;
    case (scan1_prog)
4'b0: begin              // 0
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX0;
    end
4'b0001: begin           // 1
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX1;
    end
4'b0010: begin           // 2
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX2;
    end
4'b0011: begin           // 3
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX3;
    end
4'b0100: begin           // 4
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX4;
    end
4'b0101: begin           // 5
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX5;
    end
4'b0110: begin           // 6
        scan1_prog1_display = HEX0;
        scan1_prog2_display = HEX6;
    end
4'b0111: begin           // 7
        scan1_prog1_display = HEX0;

```

```

        scan1_prog2_display = HEX7;
    end
4'b1000: begin // 8
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX8;
end
4'b1001: begin // 9
    scan1_prog1_display = HEX0;
    scan1_prog2_display = HEX9;
end
4'b1010: begin // 10
    scan1_prog1_display = HEX1;
    scan1_prog2_display = HEX0;
end
default: begin
    scan1_prog1_display = HEXOFF;
    scan1_prog2_display = HEXOFF;
end
endcase
end
default: begin
    scan1_state_display = HEXOFF;
    scan1_prog1_display = HEXOFF;
    scan1_prog2_display = HEXOFF;
end
endcase

case (scan2_state)
    lowPower: begin
        scan2_state_display = HEXOFF;
        scan2_prog1_display = HEXOFF;
        scan2_prog2_display = HEXOFF;
    end
    standby: begin
        scan2_state_display = HEXb;
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX0;
    end
    scanning: begin
        scan2_state_display = HEXS;
        case (scan2_prog)
            4'b0: begin // 0
                scan2_prog1_display = HEX0;
                scan2_prog2_display = HEX0;
            end
            4'b0001: begin // 1
                scan2_prog1_display = HEX0;
                scan2_prog2_display = HEX1;
            end
            4'b0010: begin // 2
                scan2_prog1_display = HEX0;
                scan2_prog2_display = HEX2;
            end
            4'b0011: begin // 3
                scan2_prog1_display = HEX0;
                scan2_prog2_display = HEX3;
            end
            4'b0100: begin // 4
                scan2_prog1_display = HEX0;

```

```

        scan2_prog2_display = HEX4;
    end
4'b0101: begin // 5
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX5;
end
4'b0110: begin // 6
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX6;
end
4'b0111: begin // 7
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX7;
end
4'b1000: begin // 8
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX8;
end
4'b1001: begin // 9
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX9;
end
4'b1010: begin // 10
    scan2_prog1_display = HEX1;
    scan2_prog2_display = HEX0;
end
default: begin
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX0;
end
endcase
end
idle: begin
    scan2_state_display = HEXd;
    scan2_prog1_display = HEX1;
    scan2_prog2_display = HEX0;
end
xferring: begin
    scan2_state_display = HEXt;
    case (scan2_prog)
    4'b0: begin // 0
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX0;
    end
    4'b0001: begin // 1
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX1;
    end
    4'b0010: begin // 2
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX2;
    end
    4'b0011: begin // 3
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX3;
    end
    4'b0100: begin // 4
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX4;
    end

```

```

        end
4'b0101: begin           // 5
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX5;
end
4'b0110: begin           // 6
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX6;
end
4'b0111: begin           // 7
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX7;
end
4'b1000: begin           // 8
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX8;
end
4'b1001: begin           // 9
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX9;
end
4'b1010: begin           // 10
    scan2_prog1_display = HEX1;
    scan2_prog2_display = HEX0;
end
default: begin
    scan2_prog1_display = HEX0;
    scan2_prog2_display = HEX0;
end
endcase
end
flushing: begin
    scan2_state_display = HEXF;
    case (scan2_prog)
4'b0:   begin           // 0
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX0;
    end
4'b0001: begin           // 1
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX1;
    end
4'b0010: begin           // 2
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX2;
    end
4'b0011: begin           // 3
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX3;
    end
4'b0100: begin           // 4
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX4;
    end
4'b0101: begin           // 5
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX5;
    end
4'b0110: begin           // 6

```

```

        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX6;
    end
    4'b0111: begin // 7
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX7;
    end
    4'b1000: begin // 8
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX8;
    end
    4'b1001: begin // 9
        scan2_prog1_display = HEX0;
        scan2_prog2_display = HEX9;
    end
    4'b1010: begin // 10
        scan2_prog1_display = HEX1;
        scan2_prog2_display = HEX0;
    end
    default: begin
        scan2_prog1_display = HEXOFF;
        scan2_prog2_display = HEXOFF;
    end
endcase
end
default: begin
    scan2_state_display = HEXOFF;
    scan2_prog1_display = HEXOFF;
    scan2_prog2_display = HEXOFF;
end
endcase
end
endmodule

```

```

`include "overall.v"
module overall_testbench();
    reg clk, reset;
    reg initialOn, startTransfer;
    wire [6:0] scan1_prog1_display, scan1_prog2_display, scan2_prog1_display,
        scan2_prog2_display, scan1_state_display, scan2_state_display;
    wire [3:0] scan1_prog, scan2_prog;
    wire [2:0] scan1_state, scan2_state;
    wire scan1_readyToTransfer, scan2_readyToTransfer;

    // set up clock
    parameter CLOCK_PERIOD = 10;
    initial clk = 0;
    always begin
        #(CLOCK_PERIOD/2);
        clk = ~clk;
    end

    overall dut (.scan1_state(scan1_state), .scan1_prog(scan1_prog),
        .scan2_state(scan2_state), .scan2_prog(scan2_prog),
        .scan1_state_display(scan1_state_display),
        .scan1_prog1_display(scan1_prog1_display),
        .scan1_prog2_display(scan1_prog2_display),
        .scan1_readyToTransfer(scan1_readyToTransfer),

```


[illegible]

[illegible]

[illegible]

[illegible]

[illegible]

6.1.2 iverilog & gtkwave waveforms



Figure 1: counter module waveform

 


Figure 2: counterCtrl module waveform

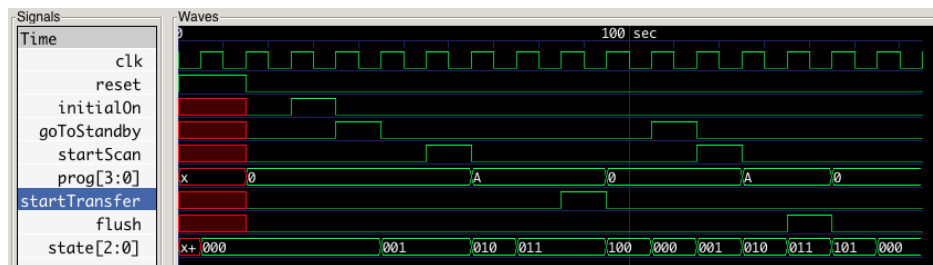


Figure 3: scannerState module waveform

 


Figure 4: scanner module waveform



Figure 5: overall module waveform

6.1.3 Signal Tap II data

6.2 C Program

```

/* Jun Park, Dawn Liang, William Li
   EE371 Lab3 Propagation Delay Calculator
   Displays total propagation delay caused
   by trace lengths and logic devices.
*/
#include <stdio.h>
#include <stdlib.h>

int main() {
    printf("Propagation Delay Calculator\n");
    printf("Definitions:\n");
    printf("There is 16 ps of delay per 0.1 inches of trace.\n");
    printf("There is 0.1 inches of trace between logic devices.\n");
}

```

```

printf("Each logic device has a 5 ns delay or 5000 ps delay.\n");
printf("\n");
printf("Number of logic devices in the signal path?");
char *p, s[100];
int gates;
while (fgets(s, sizeof(s), stdin)) { // re-prompt until non-negative integer
    gates = strtol(s, &p, 10);
    if (p == s || *p != '\n') {
        printf("Please enter a non-negative integer1: ");
    } else if (gates < 0) {
        printf("Please enter a non-negative integer2: ");
    } else {
        break;
    }
}
int totalDelay;
if (gates == 0) {
    totalDelay = 0;
} else {
    totalDelay = gates*5000 + (gates-1)*18;
}
printf("\n");
printf("Total Propagation Delay: %dps\n", totalDelay);
printf("Or equivalent to : %.3lfns\n", (totalDelay/1000.0));
return 0;
}

```

```

/* Jun Park, Dawn Liang, William Li
EE371 Lab3 Temperature Calculator
Displays Fahrenheit, Celsius, and Kelvin
*/
#include <stdio.h>
int main() {
    char scale;
    while (scale != 'f' || scale != 'F' || scale != 'c' || scale != 'C' || scale !=
        'k' || scale != 'K') {
        printf("Temperature scale(C, F, or K)?");
        scanf("%c", &scale);
        if (scale == 'f' || scale == 'F' || scale == 'c' || scale == 'C' || scale ==
            'k' || scale == 'K') {
            break;
        } else {
            printf("Scale you entered was not a valid scale. Try again.\n");
        }
    }
    double temperature;
    printf("Temperature?");
    while (scanf("%lf", &temperature) != 1) {
        scanf("%*s"); //ignore the non-double value
        printf("Temperature you entered was not valid. Try again.\n");
        printf("Temperature?");
        if (scanf("%lf", &temperature) == 1) {
            break;
        }
    }
    printf("\n");
    double tempC;
    double tempF;

```

```

double tempK;
if (scale == 'f' || scale == 'F') { //Converts F to C and K
    tempF = temperature;
    tempC = (tempF-32.0) * (5.0/9.0);
    tempK = tempC + 273.15;
} else if (scale == 'c' || scale == 'C') { //Converts C to F and K
    tempC = temperature;
    tempK = tempC + 273.15;
    tempF = tempC*(9.0/5.0) + 32;
} else { //(scale == 'k' || scale == 'K') //Converts K to F and C
    tempK = temperature;
    tempC = tempK - 273.15;
    tempF = tempC*(9.0/5.0) + 32;
}
printf("Temperature in Fahrenheit: %.2f degrees\n", tempF);
printf("Temperature in Celsius : %.2f degrees\n", tempC);
printf("Temperature in Kelvin : %.2f degrees\n", tempK);
return 0;
}

```

```

"C:\Users\Admin\Desktop\ee 371 peckol\lab3\lab3\bin\Debug\lab3.exe"
Propagation Delay Calculator
Definitions:
There is 16 ps of delay per 0.1 inches of trace.
There is 0.1 inches of trace between logic devices.
Each logic device has a 5 ns delay or 5000 ps delay.

Number of logic devices in the signal path?-9
Please enter a non-negative integer2: 3.5
Please enter a non-negative integer1: 4

Total Propagation Delay: 20054ps
Or equivalent to : 20.054ns

Process returned 0 (0x0) execution time : 11.419 s
Press any key to continue.

```

Figure 6: Output of calculateDelay program

```
"C:\Users\Admin\Desktop\ee 371 peckol\lab3\lab3\bin\Debug\lab3.exe"
Temperature scale(C, F, or K)?r
Scale you entered was not a valid scale. Try again.
Temperature scale(C, F, or K)?f
Temperature?y
Temperature you entered was not valid. Try again.
Temperature?32

Temperature in Fahrenheit: 32.00 degrees
Temperature in Celsius    : 0.00 degrees
Temperature in Kelvin     : 273.15 degrees

Process returned 0 (0x0)   execution time : 14.992 s
Press any key to continue.
```

Figure 7: Output of temperature program