

Finite State Machines

Introduction

We've looked at fundamental building blocks
Found in embedded systems designs
Now want to briefly review control of such systems

Control component typically expressed as
Finite state machine
Collection of such machines
Such devices form basis for control
Most modern computing and control systems

Fundamental Mealy and Moore models
Adequate for
Introducing FSM concepts
Expressing and implementing small designs

Expressive power limited for larger systems
Combinational explosion
When trying to develop input equations
Quickly limits utility

Basic concepts however do carry forward
Have wide application

Will first do quick review of basic concepts
Then explore how we can put them to work

Implementation of FSM may be in hardware or software

Hardware implementation of such machines

- LSI
- Arrayed logic
- PLD
- ROM
- Discrete logic

Earlier in our studies

We've looked at the basic storage element
Some simple counting and dividing circuits

Simple state machines

Like counter, divider, timer

Have

No inputs other than clock

Only primitive outputs

Such machines referred to as *autonomous clock*

We have classed such basic machines as part of datapath

In some applications can also be considered as part of control

As we move to more complex designs

Introduce

Inputs


Outputs offering rich functionality

Such functionality based upon

State of the machine

Inputs to the machine

 Our high-level block diagram begins with following



Now we have

Set of inputs

Set of outputs

Important to recognize

Outputs may be

State variables

Combinations of state variables

Combinations of

State variables

Inputs


Let's increase the level of detail of our state machine

We'll reflect the

Inputs

State variables

Outputs

 

We see that our state variables

Fed back as inputs to our system

We're now looking at the essence of the strength of the machine

It has the ability to

Recognize the state that it is in

Based upon the values of the state variables

React based upon that information

Decision as to which state to go to next now based upon


The current input
The state that the machine is currently in

Let's continue increasing the level of detail
We'll increase our view to now include
Storage elements comprising the machine
Combinational logic
Implements output functionality
Input equations to storage elements

Our block diagram now becomes

We now see that we have
n inputs
m outputs
p state variables

 Associated with each state variable
We have a memory device
At this point we do not specify the particular type



Working from this model
We can begin to formalize our model of the finite state machine

Our model must reflect
Inputs
Outputs
Which may be a function of
Inputs and State variables
State variables alone
State variables
Movement between states

Finite State Model

Finite State Machine

Also known as finite automaton
Abstract model describing
Sequential machine

Forms basis for understanding and developing
Various computational structures

We now formally define such a finite state machine

We specify the variables

X_i - Represent system n inputs

Z_j - Represent system m outputs

Y_k - Represent internal p state variables

We define our finite state machine as a quintuple

$M = \{ I, O, S, \delta, \lambda \}$

I - Finite nonempty set or vector of inputs

O - Finite nonempty set or vector of outputs

S - Finite nonempty set or vector of states

δ - Mapping $I \times S \rightarrow S$

λ_1 - Mapping $I \times S \rightarrow O$ - Mealy Machine

λ_2 - Mapping $S \rightarrow O$ - Moore Machine

\times is the Cartesian or cross product

The Cartesian product of two vectors

Gives matrix of all possible pairs

Among elements of two vectors

To reflect the different ways of expressing our output

We define

Mealy machine - λ_1

Output function of

Present state and inputs

Moore machine - λ_2

Output function of

Present state only

Putting State Machines to Work

Let's take a detailed look at how we can begin to use our model

We'll begin with a simple pattern or sequence detector

Couple of possible uses for such a system

Communications systems

Synchronize or lock onto incoming data stream

Based upon initial or synchronizing pattern

CD or DVD player

Similarly using synchronizing pattern to

Sync local timing system to data being read from device

Permit accurate sampling


We will accept data coming into our system
Data will come in serially
One bit at a time
Our specifications require
We detect the pattern 1010 in the data
If we recognize the pattern
We are to output a found signal

The immediate implication of specification
Time is an important component of our design

Let's start to analyze the problem
High-level system requirements
Input
One input
Serial stream of data
Output
One output
Logical 1 every time sequence 1010 detected

As a first step
We try to capture the requirements in a block diagram
Will begin at very high level
Intent is to capture most important details
Abstract remainder away

 For this problem we have the following simple diagram



Two alternate fundamental algorithms apply to such detection problems

For n bit pattern

1. Use n bit block window
collect n bits as working set
repeat
if working set matches pattern
succeed
else
build new working set by moving window n bit positions to left
until done

2. Use n bit sliding window
 - collect n bits as working set
 - repeat
 - if working set matches pattern
 - succeed
 - else
 - build new working set by moving window 1 bit position to left
 - until done

Next we formally express the behaviour of the system

Capture such behaviour in *state diagram*

Such a diagram

Expresses the behaviour of the system in time

Identifies each legal state of the system

Depicts means by which system got to each state

State Diagram

State diagram derives from field of mathematics called Graph Theory

State diagram and graph equivalent

Basic components of graph

Vertices

Arcs

Vertices

Each state in machine

Corresponds vertex in state diagram

Each vertex in the diagram

Corresponds to state in system

If the system has 10 states

We will have 10 vertices

Arcs

Arcs interconnect Vertices

Arcs may be

Undirected

Have no specific orientation

Undirected graph

Directed

Have specific orientation

Directed graph

Cyclic and Acyclic Graphs

Many classes of graph

Two important classes

Cyclic and *acyclic*

Cyclic

Can have closed path or cycle

From one vertex

Through several other vertices

Back to original vertex

Commonly found in flow of control applications

Acyclic

Does not have closed path or cycle

Unidirectional path(s) through graph

Building a Graph

Work with *directed cyclic graph*

Set of vertices to represent states

Will have finite number of states – *Finite State Machine - FSM*

Finite number of vertices

Set of arcs to represent transitions between states

Finite number of arcs

For each vertex

We have

2^p directed arcs

One for each combination of inputs

Arcs correspond to state transitions

Caused by input variables

These arcs express the mapping we saw earlier

$I \times S \rightarrow S$

If we have 3 inputs to system

Each state will have 2^3 arcs leaving

One arc for each possible input combination

This is where Mealy and Moore machines

Begin to run into trouble

Many systems – even if reduced

Have many more than 4 inputs


A system with 6 inputs would have

64 arcs leaving each state

Independent of whether such transitions are meaningful

For Mealy machine
 Each directed arc
 Labeled with
 Input combination
 Caused transition
 Resulting output symbol that is generated
 Associated with each arc we write
 input / output

 For Moore machine
 Directed arcs
 Unlabeled
 Within circle representing each state
 Identify output set for that state
 Illustrated in accompanying diagram
 State with 5 outputs



Behaviour

Graph or State diagram describes our system
 It shows
 Succession of states – vertices
 Through which sequential machine passes
 Output sequence which it produces
 Path(s) – arcs
 Expressing succession of states
 Interconnecting states

In many systems we can define two distinguished states

Initial State

State of machine prior to application of input sequence

Final State

State of machine after application of input sequence

Let's see what the state diagram for our system will look like

Before we can begin

 Need to clarify the specification

Consider that we receive the sequence10101010....

As noted above we have two possible interpretations

1. We examine the pattern in groups of 4

 If we detect the pattern

 We must start over looking for the pattern again

 For the above sequence

 We will detect the pattern twice

2. We can reuse part of the pattern through a sliding window
For the above pattern
We will detect the pattern 3 times

We will build the second interpretation as a Mealy machine

We begin in the *idle* state

Most of our designs use an initial or idle state

We will label that state as state A

Since we only have a single input

We will only have two arcs emanating from each state

From the idle state – we're at t_0

Our input can be either a 0 or a 1

If we get a 0

We will go to state B

Says that we now have 1 bit correct

If we get a 1


We remain in state A

Says that we have no bits correct

Our state diagram becomes

Observe that we label each arc

Showing input and output combination

 

From state B - we're at t_1

Once again our input can be either a 0 or a 1

If we get a 0

We remain in state B


Says that we still only have 1 bit correct

If we get a 1

We go to state C

Says that we have two bits correct

Our state diagram becomes

 

Observe that our output remains a 0

It must since we have not detected the full sequence yet

From state C – we're at t_2

Once again our input can be either a 0 or a 1

If we get a 0

We're winning – we go to state C

Says that we now have 3 bits correct

If we get a 1


We fail and must return to A

Says that we have no bits correct

Our state diagram becomes

Observe that our output remains a 0

 It must since we have not detected the full sequence yet



Now we're looking for the 4th bit

From state D – we're at t_3

Yet again our input can be either a 0 or a 1

If we get a 0

We're only partially win – we go to state B

Says that we now have just 2 bits correct

If we get a 1

We return to C and output a 1

Says that


We have matched the patterns

Also we still have three bits correct

Our final state diagram becomes

We have now captured in graphical presentation

Complete behaviour of our system

 

We can use such a diagram for discussion and analysis

Need somewhat different format

To begin next stage of design

The State Table

The state table contains exactly *same information* as state diagram

Expresses in tabular form

Easier to develop logic equations from

Let's take a look

A state table has

Two major subdivisions

One column

Showing the state of the system at time t_n

A set of columns

Showing the state of the system at time t_{n+1}

Each column reflects the next state for each specific input combination

Thus in general we have

p columns

One for each combination of input symbols in set I

n rows

One for each state in S

This is now the matrix we referred to earlier

The columns give us the input combinations

The rows give us the set of present and next states

To implement machine will require

k memory elements

k is smallest integer value such that

$$k \geq \log_2 n$$

For our design

We will have two columns

One for the input data taking a value of logical 0

One for the input data taking a value of logical 1

We will have 4 rows

One for each state

Taking the information directly from the state diagram we have

Present State $t = t_n$	Next State $t = t_{n+1}$	
	x = 0	x = 1
A	B, 0	A, 0
B	B, 0	C, 0
C	D, 0	A, 0
D	B, 0	C, 1

The Output Table

The next step in our process is to specify the outputs from our system

These appear in an *output table*

Once again this information

Captured directly from the state diagram

Often we will combine the state and output tables into single table

The output table has

p columns

One for each combination of input symbols in set I

n rows

One for each state in S

The output table gives us our output matrix

Here we have

- $I \times S \rightarrow O$
- $S \rightarrow O$

For each combination of input symbol and present state

Specifies output of system

Remember

If building a Moore machine

Each output column will have same value

Once again reading directly from the state diagram

The output table for our design is given as

Present State $t = t_n$	Output $t = t_{n+1}$	
	x = 0	x = 1
A	0	0
B	0	0
C	0	0
D	0	1

State Assignment

Our next step is to

Choose state variables

Assign appropriate combinations to each state

Let's us uniquely identify each state in our system

Selecting state assignment

Important step in design of finite state machine

There are wide variety of techniques of varying degrees of complexity

Let's look at four

1. Binary Assignment

Easiest is to simply use binary sequence

Initial state gets pattern of binary 0

Typically 0 chosen as value for initial state

At power on or when necessary

Storage elements in system reset by master reset signal

Reset forces output of elements to 0
Thus 0 is natural state

Each subsequent state gets next binary number

Often works with no problem

One major limitation

Building outputs as combinational patterns

Because of hazards and races associated with combinational logic

With such an approach

Run risk of having decoding spikes on our outputs

If output signals utilized to

Clock, strobe, gate, or enable

Other devices

Can have significant problems

2. Gray Assignment

One method to address problem of race conditions and hazards

Ensure that we have only single variable change between states

Reduces chances of decoding spikes

As first step

We develop table listing all states

For each state

Identify

Preceding states

Next states

For our system we have

Previous	Present	Next
C	A	B
A,D	B	C
B,D	C	A,D
C	D	B,C

Then we assign states such that

Single variable change

Previous to present

Present to next

Not always able to do

Using a Karnaugh map helps

For our system

We have 4 states

Requires we use 2 state variables

Thus we now have

M	0	1	N
0	A	B	
1	D	C	

Our state assignment now becomes

	M	N
A	0	0
B	0	1
C	1	1
D	1	0

Generally we select our initial state to have the value of binary 0
Simplifies ensuring system starts in known state

Not always possible to ensure that all adjacencies satisfied
Under such circumstances
Work to satisfy necessary ones

Based upon implementation

Implication on next two schemes

Designs architected as Moore machines

Outputs function of state only

3. One Hot Code

Another method for addressing the problem of

Combinational logic hazards on output signals

Simply avoids them

With One Hot state encoding trade off

Reduced combinational logic for additional storage elements

One Hot implies that bit pattern assigned to any state

Has at most a single one and the remainder all set to 0

Of question is the initial state

If master reset sets all storage devices to 0 state

Initial state will be all 0's

Otherwise

Initial state will be assigned pattern such as

...000001

For our four state machine possible assignments might be

LMN			LMNP					
A	0	0	0	A	0	0	0	1
B	0	0	1	B	0	0	1	0
C	0	1	0	C	0	1	0	0
D	1	0	0	D	1	0	0	0

Obvious weakness of One Hot Code

For large number of states

Number of storage devices grows quite quickly

4. M of N Encoding

M of N encoding scheme

Simple variant on One Hot encoding

Rather than permitting only single one in state assignment pattern

Any M of the possible N state variables may be set to 1

Key aspect of approach

Each state variable corresponds to an output variable

Since output derives directly from state variable storage element

Cannot possibly have race conditions and hazards

Will look at example of how this might apply shortly

The Transition Table

Once we have the state assignment

We use it to construct a *transition table*

The transition table combines our state table

With the gray state assignment we just developed

We simply substitute the state variable combination for each state

Back into the state table

For our design we have

PQ	Next State	
	x = 0	x = 1
A 00	B 01	A 00
B 01	B 01	C 11
C 11	D 10	A 00
D 10	B 01	C 11

The Input Equations

We're now ready to implement the design

For the state equations

Simply follow same procedure we did earlier

For our design

We first develop the following K Maps

PQ	0	1	X
0 0	0	0	
0 1	0	1	
1 1	1	0	
1 0	0	1	P

PQ	0	1	X
0 0	1	0	
0 1	1	1	
1 1	0	0	
1 0	1	1	Q

If we choose to use D flip flops

We write the following equations from the maps

$$D_p = \bar{P}QX + PQ\bar{X} + P\bar{Q}X$$

$$D_q = \bar{P}\bar{X} + \bar{P}Q + P\bar{Q}$$

The Output Equations

The output equations follow in a similar manner

We simply use a K Map

For our design we have

PQ	0	1	X
0 0	0	0	
0 1	0	0	
1 1	0	0	
1 0	0	1	Out

$$Out = P\bar{Q}X$$

Example

System must output an 8 bit data word in two 4 bit pieces

Least significant nibble then most significant nibble

According to the following sequence.

When a *Ready* signal is received,

1. Generate a signal *E1* to output the lower 4 bits.
2. Wait τ_d then output the signal *dStrobe*.
3. Wait $2\tau_d$ then terminate the signals *E1* and *dStrobe*
4. Generate a signal *E2* to output the upper 4 bits.
5. Wait τ_d then output the signal *dStrobe*.
6. Wait $2\tau_d$ then terminate the signals *E2* and *dStrobe*

System has

Six states

S0..S5

Four inputs

POR, Ready, τ_d , $2\tau_d$

Four outputs



E1, E2, dStrobe, countEnab

Design assumes counter to time the two delay intervals

Using M of N encoding

Can specify state variable values

	L	M	N	P
S0	0	0	0	0
S1	1	0	0	0
S2	1	1	0	0
S3	1	1	0	1
S4	1	0	1	0
S5	1	0	1	1

  

For this design state variables double as following outputs

L – countEnab

M – E1

N – E2

P – dStrobe

Design Guidelines

From our work we propose the following guidelines

1. From word description of problem, form a state diagram
2. From the state diagram develop the state table
3. Check for redundant states
4. Select a state assignment
5. Develop transition and output tables
6. Develop Karnaugh map for each state variable
7. Select memory device and develop input equations from Karnaugh map
8. Develop Karnaugh map for each output variable
9. Develop output equations from Karnaugh map

Multiple Machines

When designing complex systems


Good practice to decompose into smaller pieces

We do this when

Working with object centered language

Executing functional decomposition of system

Developing hw or sw modules

 

Using such a scheme

Utilize slave machines

To implement individual pieces of functionality

Master determines when each slave is enabled

Based upon aspect of problem being executed

Consider system with 4 major tasks

Each task comprised of multiple simpler tasks

System now consists of 5 sequential machines

Master controller

4 Slave controllers

Architecture appears as illustrated in adjacent drawing

Control of slaves can be implemented in several ways

- All devices respond to main system reset
 - Enable signal going from master to each slave
- Main system reset to master
 - Reset control to each slave derives from disjunction of
 - Master reset
 - Secondary reset derived from master
 - Advantage
 - Devices held in reset state until needed

Either implementation could hold slave devices

Unpowered or in low power mode until necessary