

# EE 371 Autumn 2016 - Lab 1

William Li, Jun Park, Dawn Liang

October 16, 2016

## 1 Abstract

## 2 Introduction

This lab focuses on designing and building VHDL (Verilog Hardware Description Language) programs. We built four different types of counters (a four stage ripple up counter using gate modeling, a four stage synchronous up counter using both dataflow model and schematic entry, and a four stage synchronous Johnson up counter using the behavioural model). To build these counters, we were introduced to both Icarus Verilog (iVerilog) and GTKWave analysis. We designed the counters using iVerilog and tested the output waveforms using GTKWave analysis. We then loaded our designs onto an Altera FPGA where we then did further testing using Signal Tap II, a logic analyzer for detecting the output waveform on the FPGA. Finally, we began a brief introduction into the C programming language. We learned the basics of a C program through the CodeBlocks IDE by compiling the Project0.c file. Finally, we built a simple C car calculator program that asks for relevant input data and outputs an approximate list price for a brand new vehicle.

## 3 Designing and building VHDL applications - counters

---

```
module DFlipFlop(q, qBar, D, clk, rst);
    input D, clk, rst;
    output q, qBar;
    reg q;

    not n1 (qBar, q);
    always@ (negedge rst or posedge clk) begin
        if(!rst)
            q = 0;
        else
            q = D;
        end
    endmodule
```

---

### 3.1 Ripple up counter

---

```
/*
    4-bit ripple-up counter, implemented using D-flipflops

    Authors: William Li, Dawn Liang, Jun Park
    Date: 16 Oct 2016
```

```

*/

module rippleUpCounter(out, clk, rst);
    // declare inputs/outputs
    output logic [3:0] out;
    input logic clk, rst;
    logic Q0, Q1, Q2, Q3, clkTemp1, clkTemp2, clkTemp3, clkTemp4;

    // connect flip flops; one ff per bit
    DFlipFlop d0(.q(Q0), .qBar(clkTemp1), .D(clkTemp1), .clk(clk),
        .rst(rst));
    DFlipFlop d1(.q(Q1), .qBar(clkTemp2), .D(clkTemp2), .clk(clkTemp1),
        .rst(rst));
    DFlipFlop d2(.q(Q2), .qBar(clkTemp3), .D(clkTemp3), .clk(clkTemp2),
        .rst(rst));
    DFlipFlop d3(.q(Q3), .qBar(clkTemp4), .D(clkTemp4), .clk(clkTemp3),
        .rst(rst));

    // output logic
    assign out = {Q3, Q2, Q1, Q0}; //not {Q0, Q1, Q2, Q3};
endmodule

// provided D-ff module
module DFlipFlop(q, qBar, D, clk, rst);
    input D, clk, rst;
    output q, qBar;
    reg q;

    not n1 (qBar, q);
    always@ (negedge rst or posedge clk) begin
        if(!rst)
            q = 0;
        else
            q = D;
    end
endmodule

```

---

```

/*
    Ripple-up counter tester

    Authors: William Li, Dawn Liang, Jun Park
    Date: 16 Oct 2016
*/

`include "rippleUpCounter.v"
module rippleUpCounter_testbench;
    logic [3:0] out;
    logic clk, rst;

```

```

rippleUpCounter dut(.out, .clk, .rst);

parameter PERIOD = 100; // period = length of clock
initial begin
    clk <= 0;
    forever #(PERIOD/2) clk = ~clk;
end

initial begin
    rst=0; @(posedge clk);
    rst=1; @(posedge clk);
end
endmodule

```

---

## 3.2 Synchronous up counter

---

```

module synUpCounter(out, clk, rst);
    output logic [3:0] out;
    input logic clk, rst;

    logic Q0, Q1, Q2, Q3;
    logic D0, D1, D2, D3;

    DFlipFlop dff0(.q(Q0), .qBar(), .D(D0), .clk(clk), .rst(rst));
    DFlipFlop dff1(.q(Q1), .qBar(), .D(D1), .clk(clk), .rst(rst));
    DFlipFlop dff2(.q(Q2), .qBar(), .D(D2), .clk(clk), .rst(rst));
    DFlipFlop dff3(.q(Q3), .qBar(), .D(D3), .clk(clk), .rst(rst));

    assign D0 = (~Q0)&rst;
    assign D1 = ((Q0&~Q1) | (Q1&~Q0))&rst;
    assign D2 = ((Q2&~Q1) | (Q2&~Q0) | (Q1&Q0&~Q2))&rst;
    assign D3 = ((Q3&~Q2) | (Q3&~Q1) | (Q3&~Q0) | (~Q3&Q2&Q1&Q0))&rst;

    assign out = {Q3, Q2, Q1, Q0};
endmodule

module DFlipFlop(q, qBar, D, clk, rst);
    input D, clk, rst;
    output q, qBar;
    reg q;

    not n1 (qBar, q);
    always@ (negedge rst or posedge clk) begin
        if(!rst)
            q = 0;
        else
            q = D;
    end
endmodule

```





```

begin
    temp <= 4'b0000;
end
else if (clk == 1'b1)
begin
    temp <= {~temp[0], temp[3:1]}; // right shift and negate most
    signif bit
end
end

assign out = temp;
endmodule

module DFlipFlop(q, qBar, D, clk, rst);
input D, clk, rst;
output q, qBar;
reg q;

not n1 (qBar, q);
always@ (negedge rst or posedge clk) begin
    if(!rst)
        q = 0;
    else
        q = D;
    end
endmodule

```

---

```

module johnsonUpCounter_testbench;
    logic [3:0] out;
    logic clk, rst;

    johnsonUpCounter dut(.out, .clk, .rst);

    parameter PERIOD = 100; // period = length of clock
    initial begin
        clk <= 0;
        forever #(PERIOD/2) clk = ~clk;
    end

    initial begin
        rst=0; @(posedge clk);
        rst=1; @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
    end

```

```

        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        rst=0; @(posedge clk);
        @(posedge clk);
        @(posedge clk);
        $stop();
    end
endmodule

```

---

### 3.4 Synchronous up counter (schematic entry)

## 4 Learning the C language

---

```

#include <stdio.h>
int main(void)
{
    // declare and initialise variables
    // inputs
    float man_cost, mark_up, sales_tax, discount;

    // outputs
    float list_price = 0.0;

    printf("Car list price calculator\n\n");

    printf("Enter the manufacturer's cost ($): ");
    scanf("%f", &man_cost);

    printf("Enter the estimated markup (%): ");
    scanf("%f", &mark_up);

    printf("Enter the sales tax (%): ");
    scanf("%f", &sales_tax);

    printf("Enter the dealer's pre-tax discount (%): ");
    scanf("%f", &discount);

    printf("Manufacturer's cost = $%.2lf\n", man_cost);
    printf("Est. dealer's markup = %.2lf%%\n", mark_up);
    printf("Pre-tax discount   = %.2lf%%\n", discount);
    printf("Sales tax           = %.2lf%%\n", sales_tax);
    printf("-----\n");
}

```



```
list_price = man_cost * (1 + mark_up / 100) * (1 - discount/100) *  
            (1 + sales_tax/100);  
  
printf("Your car will cost %3.2f\n", list_price);  
  
return 0;  
}
```

---

## 5 Failure Modes Analysis